

### Examples: Noise

1. The Gain-Bandwidth of an op-amp is 6 MHz. If the gain is 100:

- a. What is the cut-off frequency if the amplifier is non-inverting?

$$f_c = \frac{GBW}{Gain} = \frac{6 \times 10^6}{100} = 60 \text{ kHz}$$

- b. What is the white noise equivalent bandwidth?

This will depend if it is non-inverting or inverting. If it is non-inverting the gain and noise gain will be the same so:

$$NEB = 1.57 \times \frac{GBW}{\text{Noise Gain}} = 1.57 \times 60 \text{ kHz} = 94.2 \text{ kHz}$$

If it is inverting the Noise Gain will be 101.

$$NEB = 1.57 \times \frac{GBW}{\text{Noise Gain}} = 1.57 \times \frac{6 \times 10^6}{101} = 93.27 \text{ kHz}$$

2. Consider Figure 1 where  $R_2=10\text{ k}\Omega$  and  $R_1=2\text{ k}\Omega$ :

a. What is the voltage gain of the amplifier?

Signal gain = -5

b. What is the noise gain of the amplifier?

Noise gain = 6

Why? Because the voltage noise is always referred to the non-inverting input.

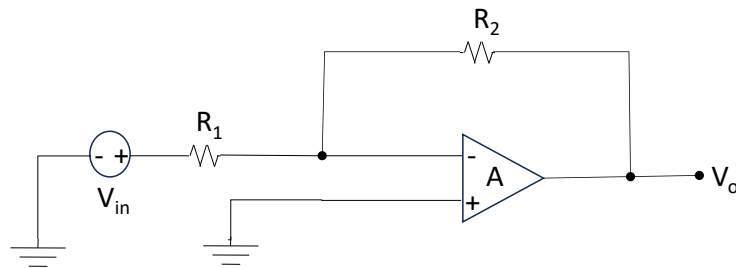


Figure 1.

3. An inverting amplifier is shown in Figure 2. The data sheet for the op-amp gives the value of Gain Bandwidth (GBW) as 5 MHz, a voltage spectral density of white noise of

$e_{nw} = 20\text{ nV} / \sqrt{\text{Hz}}$  and a current spectral density of white noise of  $i_{nw} = 0.4\text{ pA} / \sqrt{\text{Hz}}$ .

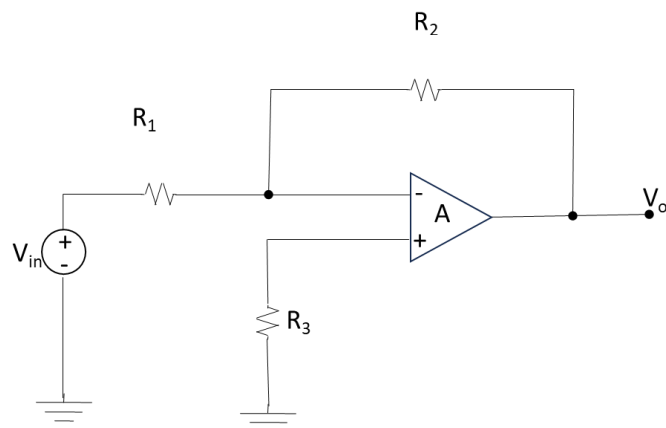


Figure 2

- a. If a gain of 100 is required and R2 is 101 kΩ calculate R1 and R3.

The gain is given by  $G = -\frac{R_2}{R_1}$  so:

$$100 = \frac{101 \text{ k}\Omega}{R_1} \text{ so:}$$

$$R_1 = 1.01 \text{ k}\Omega$$

- b. What is the noise gain?

$G_n = 101$  (Remember noise is always referred to the non-inverting input)

- c. What is the value of  $f_H$ ?

$$f_H = \frac{GBW}{G_n} = \frac{5 \times 10^6}{101} = 49.5 \text{ kHz}$$

- d. What is the value of NEB?

$$NEB = 1.57 \times 49.5 \text{ kHz} = 77.715 \text{ kHz}$$

- e. What is the thermal noise voltages at the inverting and non-inverting inputs?

$$E_3 = E_{RP} = \sqrt{4kT \times 1.57 \times f_H \times 1000} = \sqrt{4 \times 1.38 \times 10^{-23} \times 300 \times 77700 \times 1000} = 1.13 \text{ }\mu\text{V}$$

- f. What is the RMS input noise due to  $e_{nw}$ ?

$$E_n = e_{nw} \sqrt{1.57 f_H} = 20 \times 10^{-9} \sqrt{1.57 \times 49500} = 5.58 \text{ }\mu\text{V}$$

- g. What is the RMS input noise due to  $i_{nw}$ ?

$$E_{nn} = E_{np} = R_1 \parallel R_2 \times i_{nw} \sqrt{1.57 f_H} = 1000 \times 0.4 \times 10^{-12} \sqrt{1.57 \times 49500} = 111.5 \text{ nV}$$


- h. What is the total input noise?

$$E_{ni} = \sqrt{E_{RP}^2 + E_{R3}^2 + E_{nn}^2 + E_{np}^2 + E_n^2} = \sqrt{2 \times 1.2769 \times 10^{-12} + 2 \times 1.243 \times 10^{-14} + 3.114 \times 10^{-11}} = 5.8 \text{ }\mu\text{V}$$

- i. What is the output noise?

$$E_{no} = E_{ni} \times G_n = 586 \text{ }\mu\text{V}$$

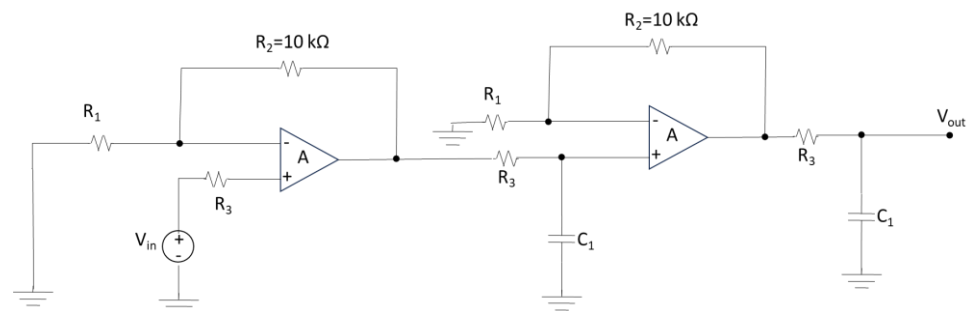4. It is proposed to use a two-stage amplifier with symmetrical lower gains for an overall gain of 100. The op amps to be used are in a single package and have a voltage spectral density of white noise,  $e_{nw}$ , of  $5nV / \sqrt{Hz}$  and a GBW of 5 MHz (note that there is negligible current spectral densities of white noise, so  $i_{nw}$  can be ignored).
- Using a feedback resistor of  $10\text{ k}\Omega$  in both stages, and inserting external low pass filters with a cut-off frequency,  $f_H$ , of 70 kHz:
    - Draw a schematic of the 2-stage amplifier and determine the component values. You should assume that the external filter provides a much lower cut-off than the closed loop bandwidth of each stage.



We should distribute the gain evenly over two stages so Gain of each stage = 10.  
Then find  $R_1$ ,  $R_3$  and  $C_1$ .

- Calculate the rms output noise. In your calculations you may assume that the input current noise is negligible, and that the temperature is  $25^\circ\text{C}$ .

The important thing to realize is that the NEB of the two stages will differ since the noise of the 1<sup>st</sup> stage will see 2 low pass filter functions.

- What is the SNR for an output voltage of 4V peak-to-peak?

Note that the output voltage is peak to peak. Need to get to rms.