



University
of Glasgow

UESTC 3003: Electronic System Design

Static Errors

Lecture 2.1: Revision of Op Amps

Dr Sajjad Hussain

Thanks to Prof. Duncan Bremner

**WORLD
CHANGING
GLASGOW**

Sajjad.Hussain.2@glasgow.ac.uk

System Engineering : Signal Conditioning



- In **Electronic System Design** we will consider how to provide the best possible input signals to the system. This means signals that are:-
 - **Accurate:** providing the most accurate signal to the system
 - **Clean:** providing the system with the cleanest, lowest noise signal
 - **Immune:** (from disturbance): signals remain accurate and clean when there is interference
- Our course will explore how to deal with low level signals and condition them for the system to use (probably in a digital process)


"Pray, Mr. Babbage, if you put into the machine wrong figures, will the right answers come out?" ... I am not able rightly to apprehend the kind of confusion of ideas that could provoke such a question.

— [Charles Babbage](#), *Passages from the Life of a Philosopher*

Source Wikipedia

Opamps Revision

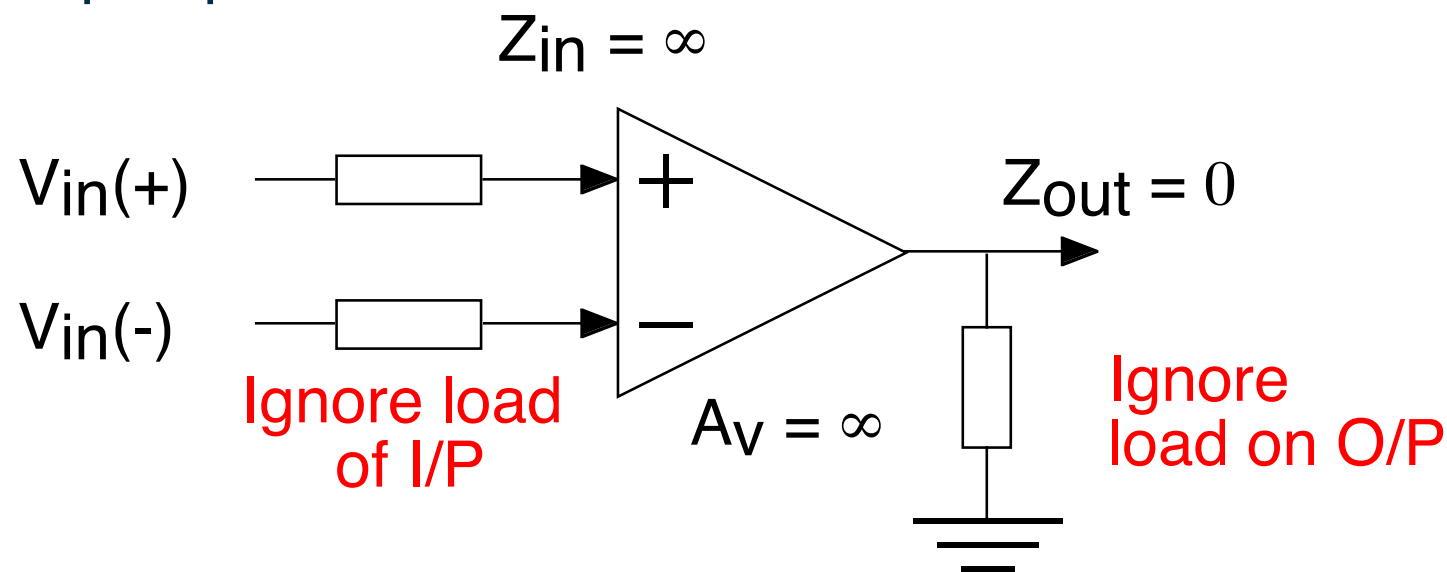
- Analogue design simplest using opamps
- Start with perfect opamp



Virtual Earth


$$V_{OUT} = \forall (V_{IN}(+) - V_{IN}(-))$$

Perfect opamp calculations (Revision)

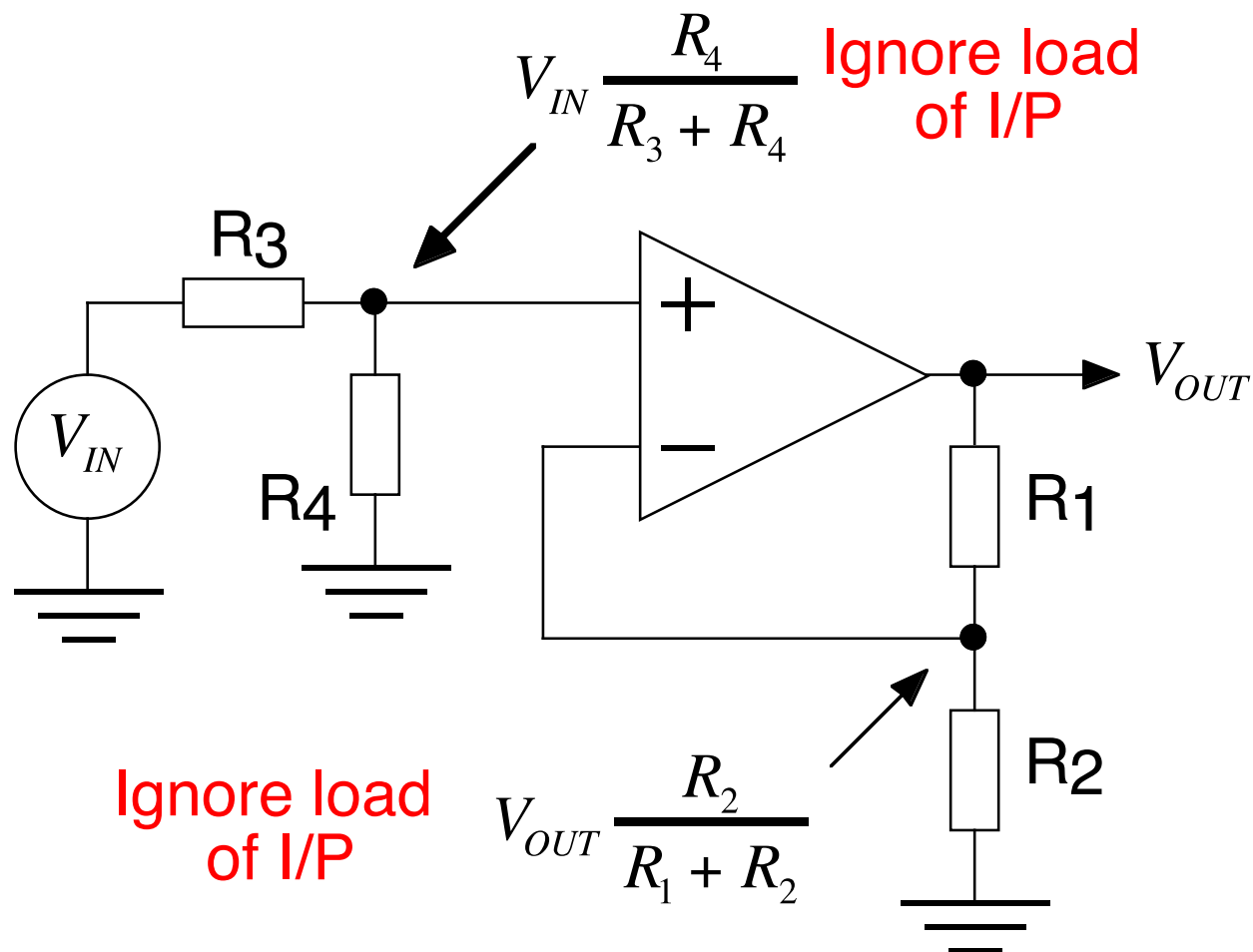




Negative Feedback

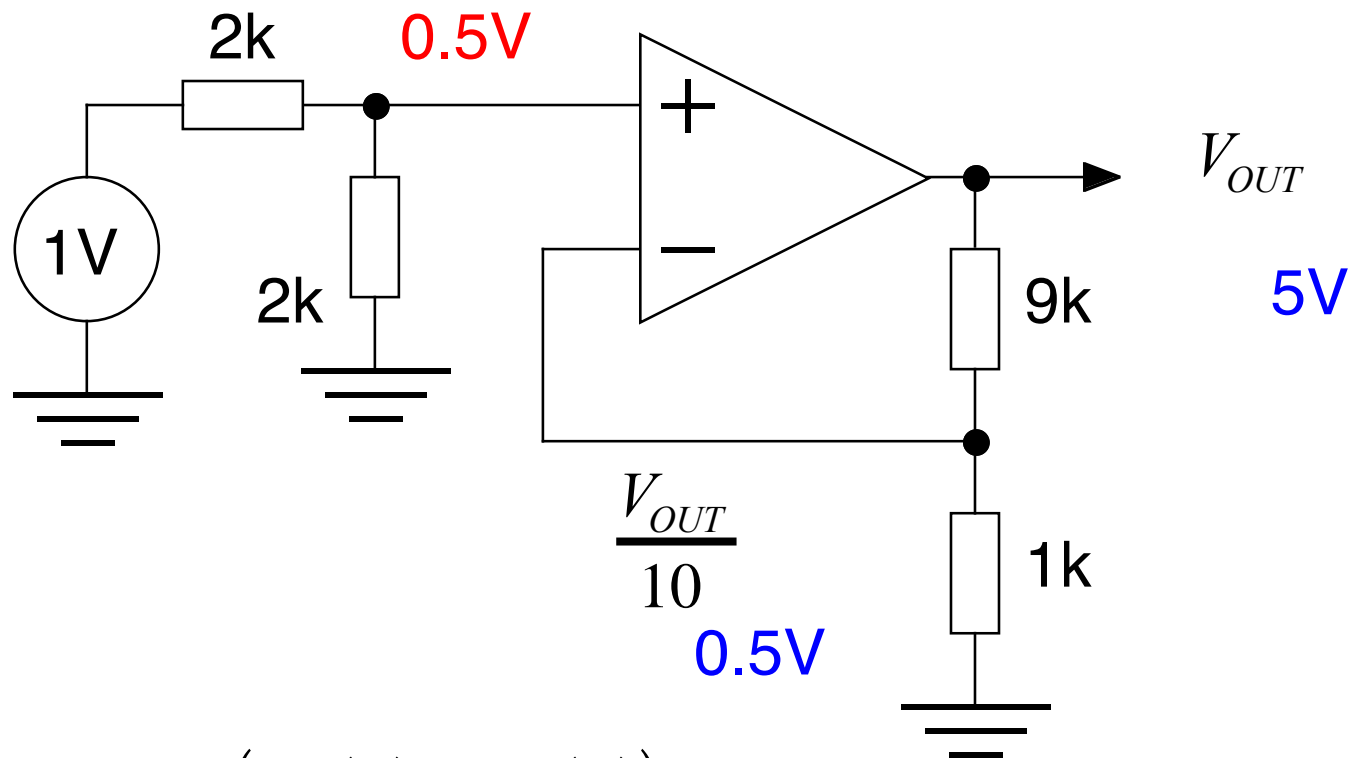

$$V_{OUT} = \infty (V_{IN}(+) - V_{IN}(-)) = \infty \cdot 0$$

- Calculate voltage at (+), (−) inputs as a function of
 - Input voltage
 - Output voltage
- Output does **whatever it takes** to make input voltages (+) & (−) equal
- Inputs do not **directly** change anything

Example 2: The Integrator

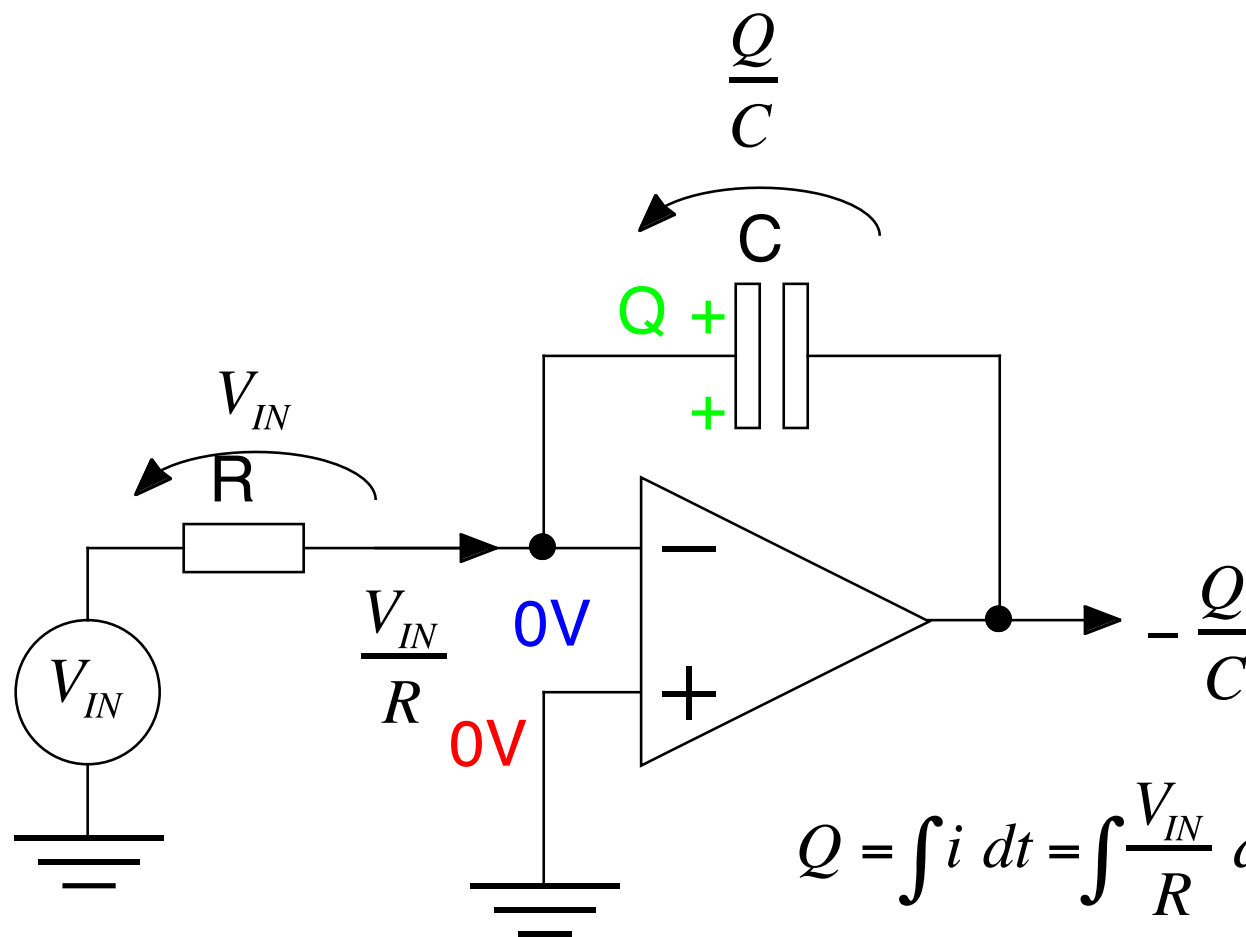


$$Q = \int i \, dt = \int \frac{V_{IN}}{R} \, dt \Rightarrow V_{OUT} = -\int \frac{V_{IN}}{CR} \, dt$$




Opamps are not perfect

- Input offset voltage
- Input currents (“Bias” and “Offset”)
- Speed
 - Gain-Bandwidth product
 - Slew Rate
- Noise
- Other
 - CMRR, R_{OUT} , PSRR, Gain, Power.....

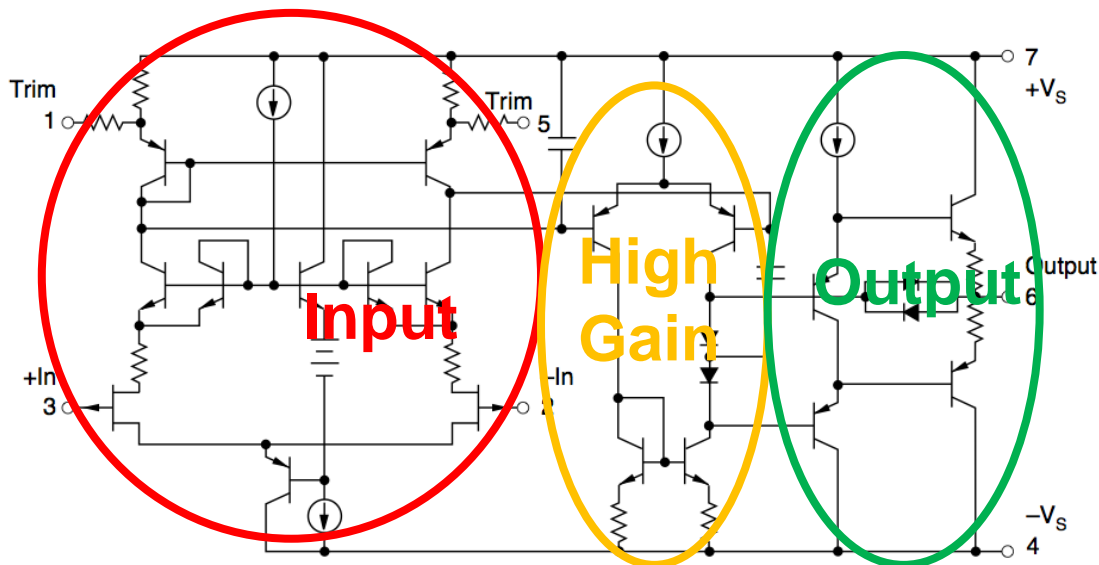⇒ **Compare (standardized)
datasheet parametrics
... (V_{os} , I_b , I_{os})**



Opamps are complicated

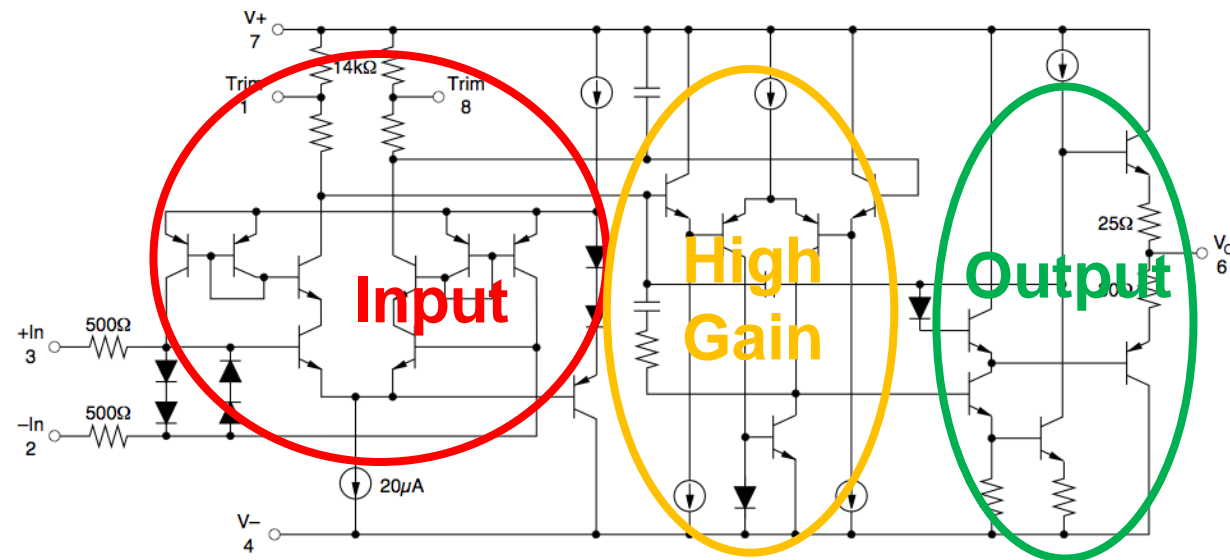

... don't try and
compare schematics;
leave that to experts!



Perfect opamp calculations are easy... *(but real opamps are more difficult...)*

Method:


- Opamps are not perfect:

Form a **model** of an imperfect opamp which is a perfect opamp
PLUS additional (ideal) voltage and current sources

- Calculations still (relatively) easy (perfect opamp plus linear components)
- Source values become optimisation parameters for system
- Different circuits can be compared using standard parameters

System Design = **Choice**

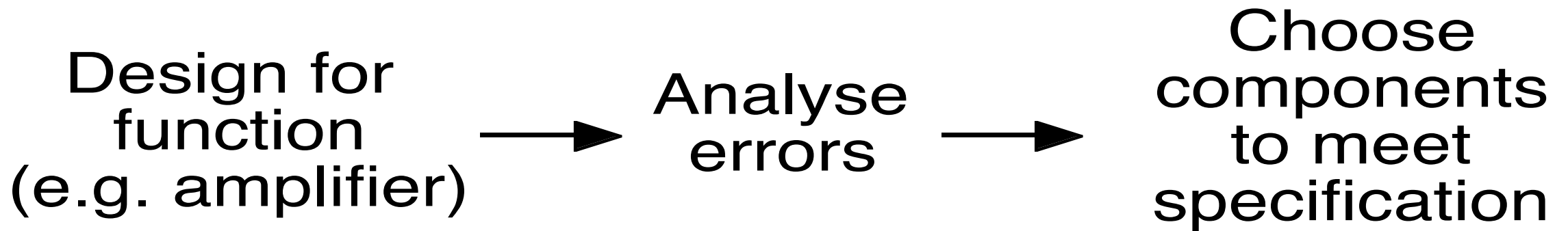- No opamp is perfect
- Choice of hundreds of different OpAmps
- Pennies (4p for a dual) -> £371 each
 - RS sell a reduced selection of the best opamps in a limited range of grades (4777)



Tools to help you...

- You **cannot** get a computer to do the design for you...
- ...but you **can** get it to check if the circuit operates the way **YOU** wanted it to
- **Simulated Circuit Programme with Integrated Circuit Emphasis (**SPICE**)**
- many different variants derived from UC Berkeley :
- PSPICE, HSPICE,
- We will use LTSpice or Orcad/PSPice
- - **It is a free download** from Linear Technology Inc (Mac & PC)
- - It consists of Schematic Capture, Simulator, and Waveform engine
- It is one of the simplest SPICE versions I have found
- <http://www.linear.com/designtools/software/#LTspice>



University
of Glasgow

Thank you
谢谢

INSPIRING
PEOPLE

#UofGWorldChangers



@UofGlasgow