

Electronic System Design 3003

Lecture: Figure of Merit

Static Errors

Dr Sajjad Hussain

Thanks to Prof. Duncan Bremner



Sajjad.Hussain.2@glasgow.ac.uk

Design example: Figures of merit

Often many numbers contribute:


Define a **Figure of merit** for the component

Figure of merit is a function of all significant contributions of the component to the total system error.

Figure of merit changes **monotonically** with the overall error due to the component

The total error contributed by the component is clearly a good choice


Example: Integrate-and-Hold

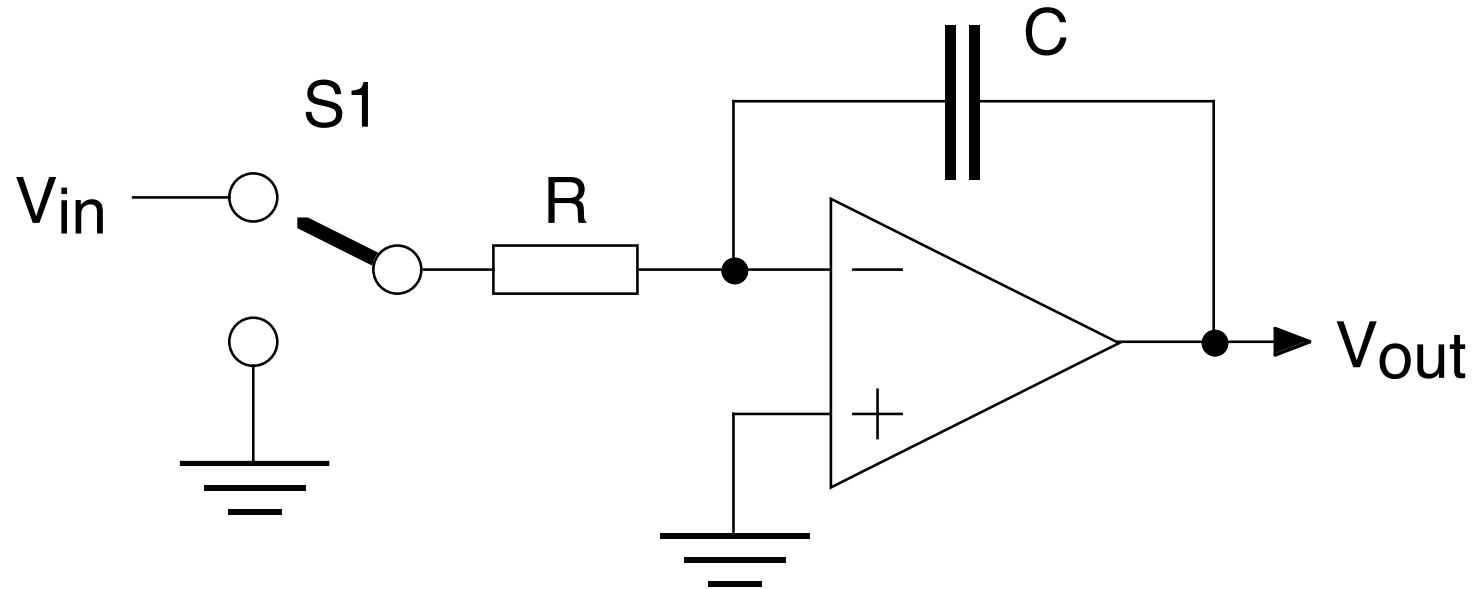

If S1 connects to V_{in} circuit is an integrator $V_{out} = - \int \frac{V_{in}}{RC} dt$

If S1 connects to 0V circuit is a memory $V_{out} = \text{constant}$

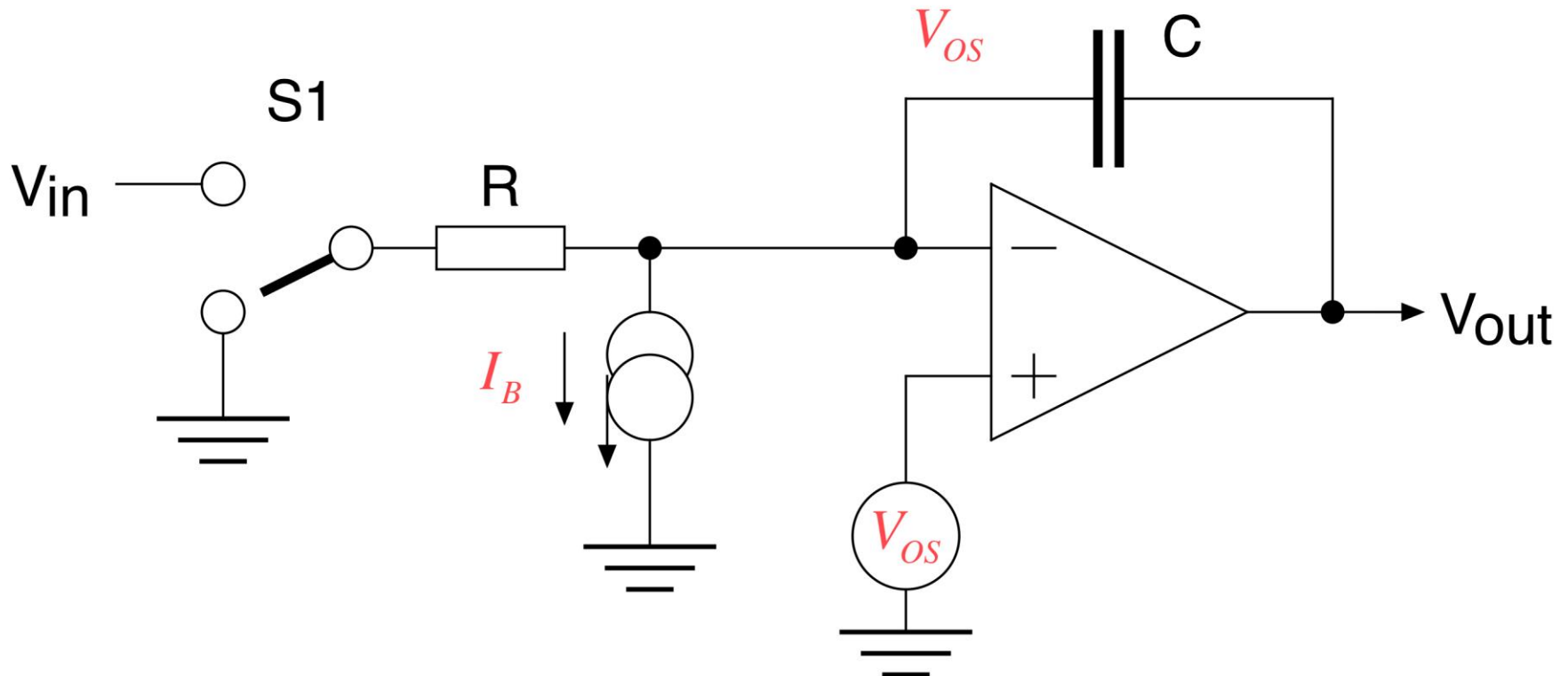Important parameter is drift during "Memory"



$$\left| \frac{dV_{out}}{dt} \right| = \frac{1}{C} \frac{dQ}{dt} = \frac{1}{C} I_B + \frac{V_{os}}{R} \frac{d}{dt}$$

Time constant is fixed: $\tau = RC$ \therefore one free parameter (R)

$$\left| \frac{dV_{\text{out}}}{dt} \right| = \frac{1}{C} \left(I_B + \frac{V_{OS}}{R} \right) = \frac{1}{\tau} (I_B R + V_{OS})$$

Optimisation: make R as small as possible

Practical limits on R:


If R too small,
Input Voltage range
is too small

Also:


- Supply current
- Power dissipation
- Thermal drift
- V across PCB
- Available C values

$$R \geq 2k\Omega$$

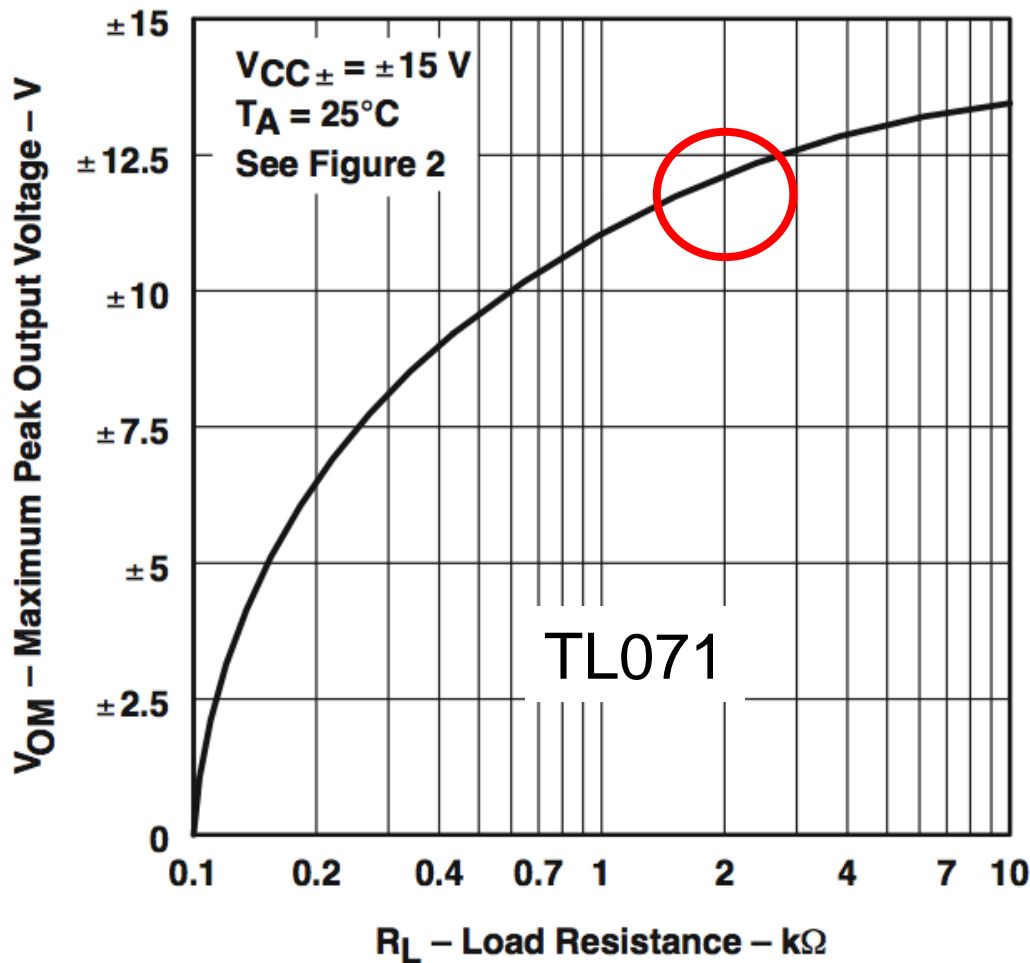MAXIMUM PEAK OUTPUT VOLTAGE
vs
LOAD RESISTANCE




Naïve circuit ($\tau=10s$)

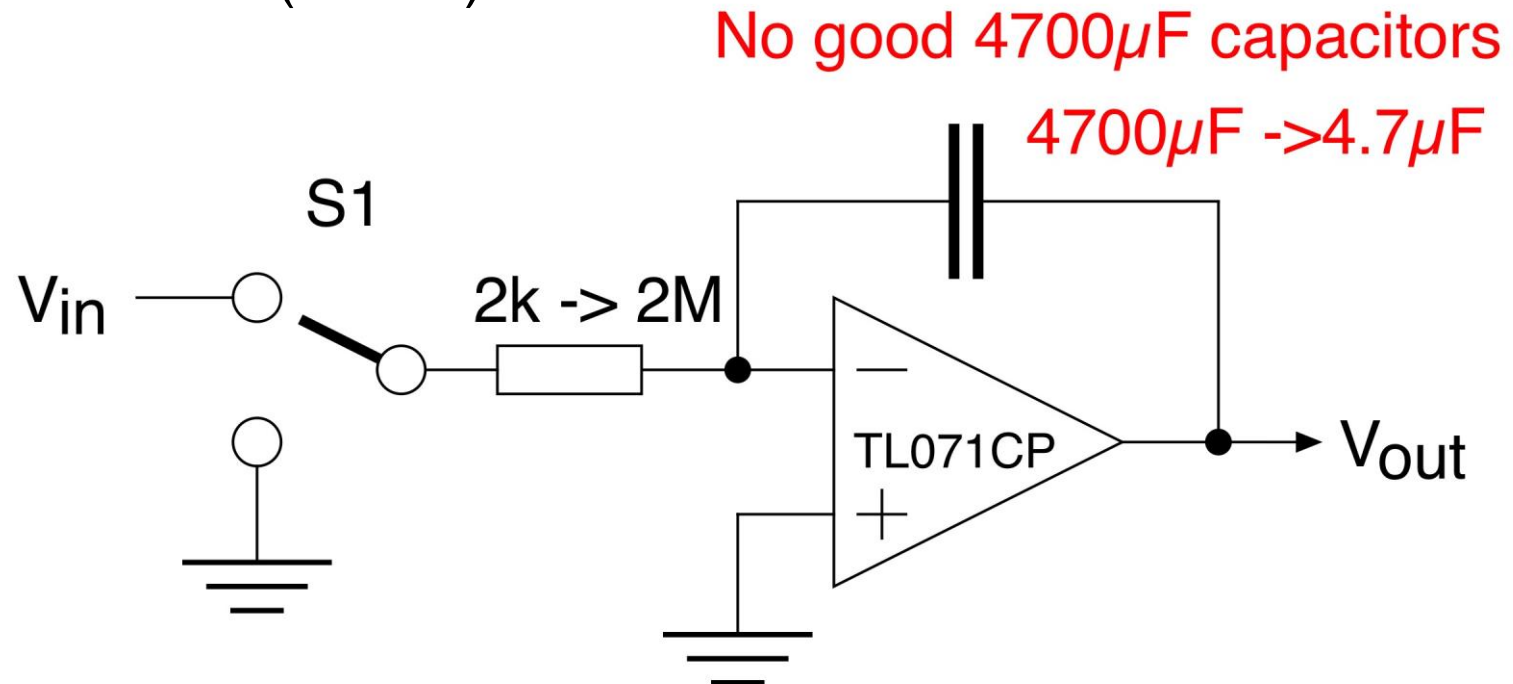


$$\left| \frac{dV_{\text{out}}}{dt} \right| = \frac{1}{\tau} (I_B R + V_{OS}) = \frac{1}{10s} \cdot (200pA \cdot 2M\Omega + 10mV) = 1.04mV \cdot s^{-1}$$

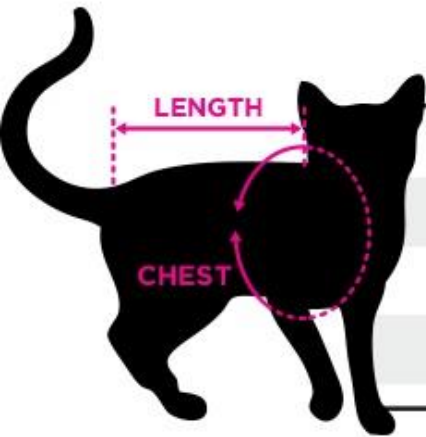How large is a 4700 μ F Polypropylene Capacitor?



	INCHES/POUNDS			CENTIMETERS/KILOGRAMS		
	SMALL	MEDIUM	LARGE	SMALL	MEDIUM	LARGE
CHEST	11-14 in	14-17 in	17-20 in	28-36 cm	36-43 cm	43-51 cm
LENGTH	10-13 in	13-16 in	13-16 in	26-33 cm	33-41 cm	33-41 cm
APPROX. WEIGHT	4-8 lbs	8-12 lbs	12-16 lbs	2-4 kg	4-6 kg	6-8 kg

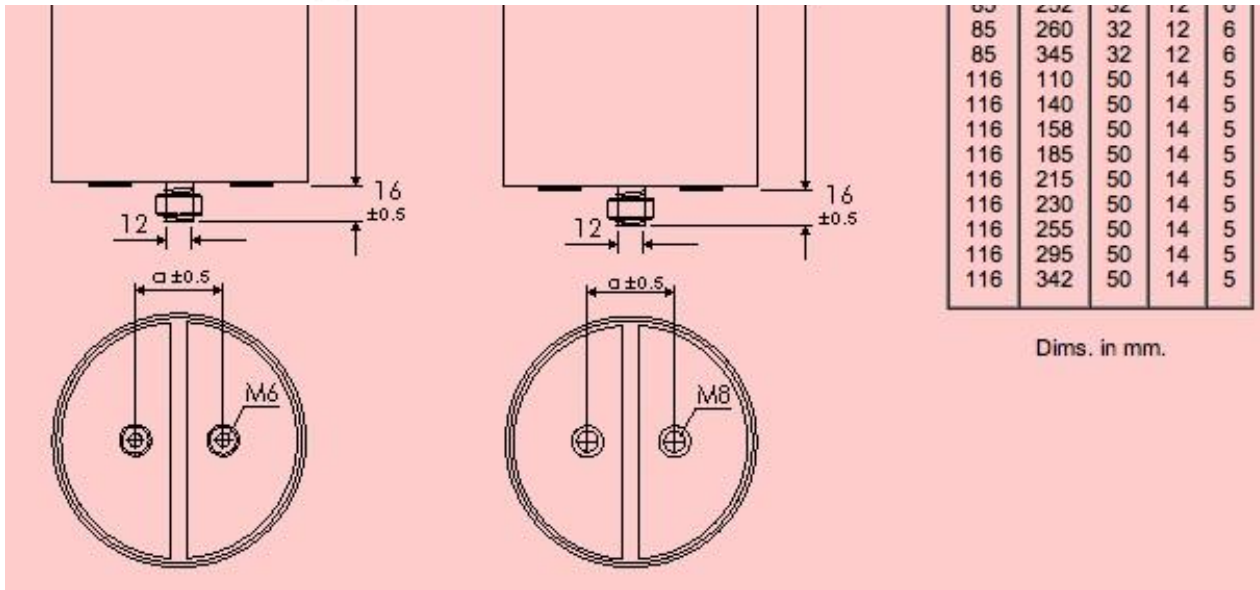

↑
This one

← This one

Electrolytic Capacitors **No!!!**
 Relatively small
 Low quality
 Poor tolerance
 Temperature sensitive
 Not ideal for precision
 circuits!

(Wima DC-LINK MKP 6 HP 4920 μ F 600V)



University
of Glasgow

Thank you
谢谢

INSPIRING
PEOPLE